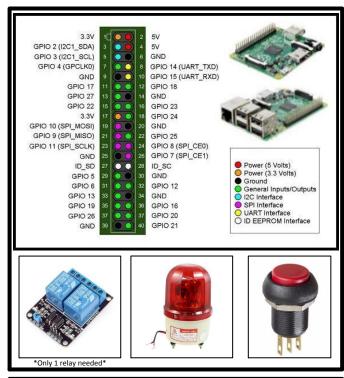
Raspberry Pi GoalLight GPIO connections and setup









Ari Mandjelikian

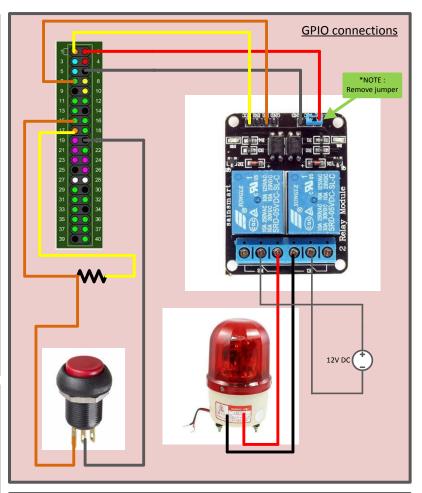To reduce the amount of plugs on the outside of the can, i decided to use a 12V power supply and add a car USB adapter to go from 12V to 5V for the Raspberry Pi inside of the can. I also added a 3.5mm audio jack extension to be able to make a hole on the can and glue the female side to it.



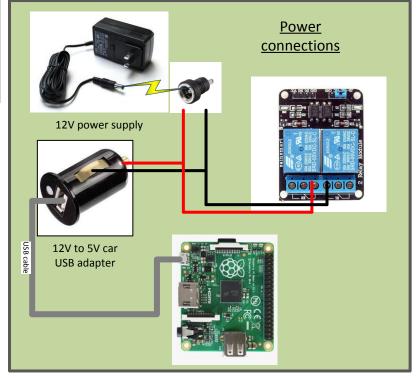

10/04/2016